

Chapter 2 — Basic Laws

Dr. Waleed Al-Hanafy

waleed_alhanafy@yahoo.com

Faculty of Electronic Engineering, Menoufia Univ., Egypt

MSA Summer Course:

Electric Circuit Analysis I (ESE 233) — Lecture no. 2

July 17, 2011

Overview

- 1 Ohm's Laws
- 2 Nodes, Branches, and Loops
- 3 Kirchhoff's Laws
- 4 Series and Parallel Resistors
- 5 Conclusions

Reference:

[1] Alexander Sadiku, Fundamentals of Electric Circuits, 4th ed. McGraw-Hill, 2009.

Resistance and Resistivity

The physical property, or ability to resist current, is known as *resistance* and is represented by the symbol R . The resistance of any material with a uniform cross-sectional area A and length l is given as

$$R = \rho \frac{l}{A}, \quad \text{ohms } (\Omega)$$

where ρ is known as the *resistivity* of the material in ohm-meters.


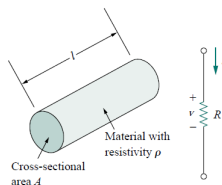



TABLE 2.1 Resistivities of common materials.

Material	Resistivity ($\Omega\cdot\text{m}$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

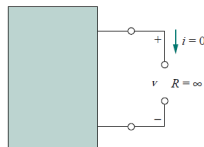

Definitions

- **Branch:** *A branch represents a single element such as a voltage source or a resistor*
- **Node:** *A node is the point of connection between two or more branches*
- **Loop:** *A loop is any closed path in a circuit*
- Two or more elements are in **series** if they are cascaded or connected sequentially and consequently carry the same current. Two or more elements are in **parallel** if they are connected to the same two nodes and consequently have the same voltage across them.

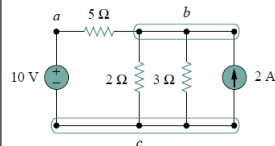

introduction


- Ohm's law by itself is not sufficient to analyse circuits. However, when it is coupled with Kirchhoff's two laws, we have a sufficient, powerful set of tools for analysing a large variety of electric circuits.
- Kirchhoff's laws were first introduced in 1847 by the German physicist *Gustav Robert Kirchhoff (1824–1887)*.
- These laws are formally known as Kirchhoff's current law (KCL) and Kirchhoff's voltage law (KVL).
 - Kirchhoff's first law (KCL) is based on the law of conservation of charge, which requires that the algebraic sum of charges within a system cannot change.
 - Kirchhoff's second law (KVL) is based on the principle of conservation of energy.

Kirchhoff's Current Law (KCL)

KCL: states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0,$$

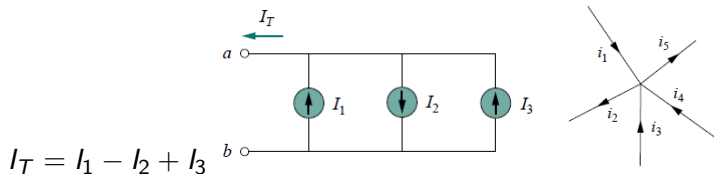where N is the number of branches connected to the node and i_n is the n th current entering (or leaving) the node.




Kirchhoff's Voltage Law (KVL)

KVL: states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0,$$

where M is the number of voltages in the loop (or the number of branches in the loop) and v_m is the m th voltage.

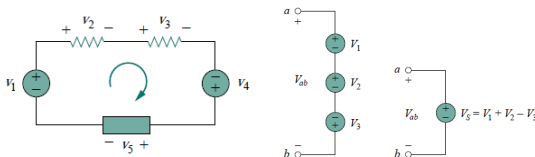Example: $-v_1 + v_2 + v_3 - v_4 + v_5 = 0$, or $v_2 + v_3 + v_5 = v_1 + v_4$,
i.e., sum of voltage drops = sum of voltage rises



Series & Voltage Division

The *equivalent resistance* of any number of resistors connected in series is the sum of the individual resistances. For N resistors in series then,

$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

Notice that the source voltage v is divided among the resistors in direct proportion to their resistances; the larger the resistance, the larger the voltage drop. This is called the *principle of voltage division*, and the circuit in Fig. 2.29 is called a *voltage divider*.

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

Parallel & Current Division

The *equivalent resistance* of two parallel resistors is equal to the product of their resistances divided by their sum.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N} \implies R_{eq} = \frac{R}{N} \quad \text{if } R_1 = R_2 = \cdots = R_N = R$$

The *equivalent conductance* of resistors connected in parallel is the sum of their individual conductances.


$$G_{eq} = G_1 + G_2 + \cdots + G_N$$

$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

Example

Find R_{eq}

Answer 14.4Ω

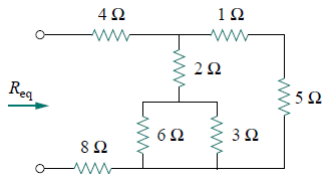

Conclusion

Concluding remarks

- Basic circuits laws are studied
- These laws include, Ohm's law, Kirchhoff's two laws
- Series and parallel connections of resistors are discussed
- Voltage and current divisions are identified as a result of series and parallel resistors connection respectively
- Some illustrative examples are given.