

Chapter 2 — Wye-Delta Transformations

Dr. Waleed Al-Hanafy

waleed_alhanafy@yahoo.com

Faculty of Electronic Engineering, Menoufia Univ., Egypt

MSA Summer Course:

Electric Circuit Analysis I (ESE 233) — **Lecture no. 3**

July 20, 2011

Overview


- 1 Introduction
- 2 Delta to Wye Conversion
- 3 Wye to Delta Conversion
- 4 Examples
- 5 Conclusions

Reference:


[1] Alexander Sadiku, Fundamentals of Electric Circuits, 4th ed. McGraw-Hill, 2009.

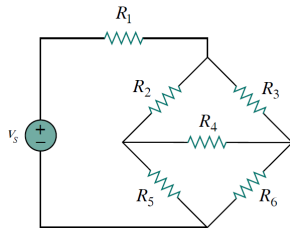Problem Statement


- Situations often arise in circuit analysis when the resistors are neither in parallel nor in series.
- For example, consider the bridge circuit shown.
- How do we combine resistors $R_1 - R_6$ when the resistors are neither in series nor in parallel?
- Many circuits of the type shown can be simplified by using three-terminal networks.
- These are the wye (Y) or tee (T) network, and the delta (Δ) or pi (Π) network as will be shown next.
- These networks occur by themselves or as part of a larger network.



Y, T, Δ , and Π Resistors Connections

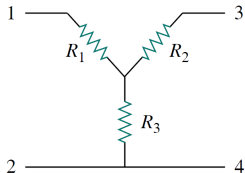


(a)

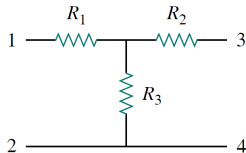


(b)

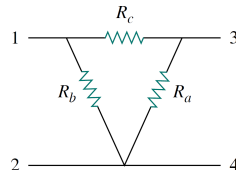Two forms of the same network: (a) Y, (b) T.



(a)

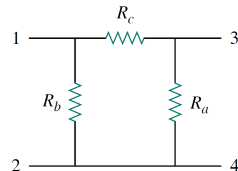

(b)


Two forms of the same network: (a) Δ , (b) Π .

Delta to Wye Conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (1)$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} \quad (2)$$
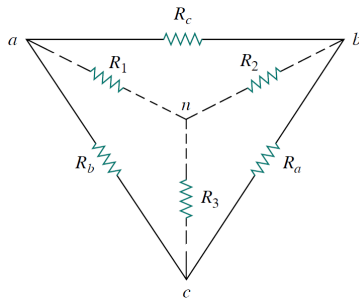
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} \quad (3)$$




Wye to Delta Conversion

$$R_a = R_2 + R_3 + \frac{R_2 R_3}{R_1} \quad (4)$$

$$R_b = R_1 + R_3 + \frac{R_1 R_3}{R_2} \quad (5)$$
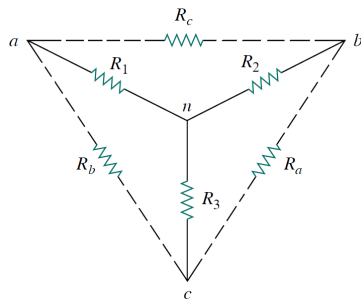
$$R_c = R_1 + R_2 + \frac{R_1 R_2}{R_3} \quad (6)$$



Special Cases: Balanced Y and Δ

If in a Y resistors connection

$$R_1 = R_2 = R_3 = R_Y \quad (7)$$

and in a Δ resistors connection

$$R_a = R_b = R_c = R_{\Delta}, \quad (8)$$


both Y and Δ networks are said to be balanced and in these cases:

$$R_Y = \frac{R_{\Delta}}{3} \quad \text{or} \quad R_{\Delta} = 3R_Y \quad (9)$$

Examples 1

1) Transform the wye network shown to a delta network.


Answer: $R_a = 140\ \Omega$, $R_b = 70\ \Omega$, $R_c = 35\ \Omega$.

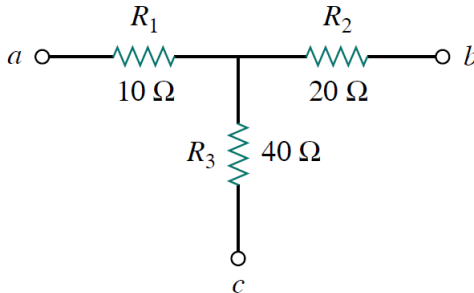

Examples 2

2) For the bridge network shown, find R_{ab} and i .


Answer: 40Ω , 2.5 A .

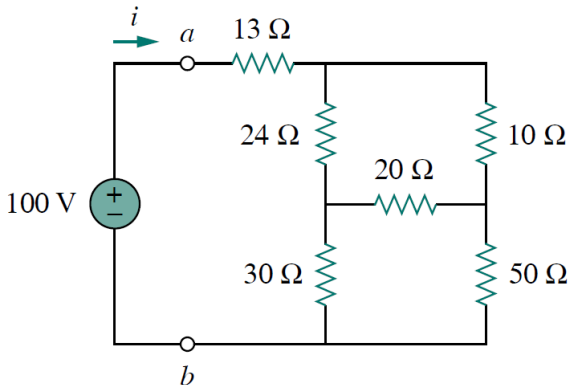

Examples 3

3) Obtain the equivalent resistance at the terminals a-b of the circuit shown.

Answer: 36.25Ω .

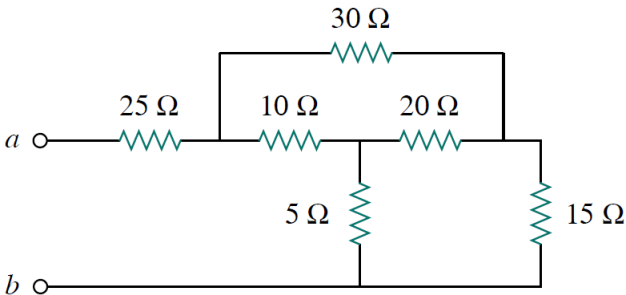

Conclusion

Concluding remarks

- In circuit analysis there are situations often arise when the resistors are neither in parallel nor in series.
- In these situations, it is very helpful to use three-terminal equivalent circuit transformations.
- These are known as Wye-Delta or Delta-Wye Transformations.
- Both cases are studied and discussed.
- Some illustrative examples are given.