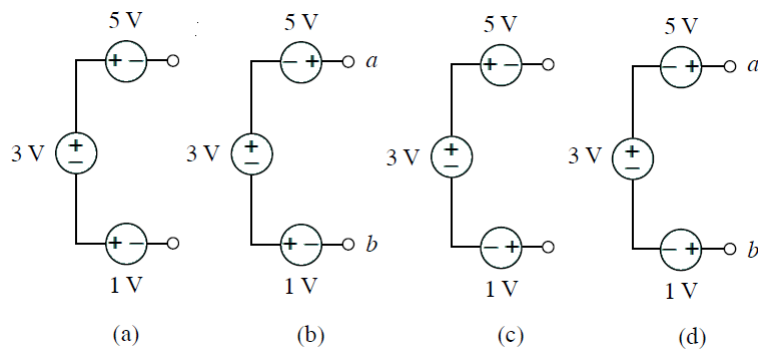


# Review Problems


## (Electric Engineering)

### Chapter 2


- 1) The voltage across a  $5\text{-k}\Omega$  resistor is  $16\text{ V}$ . Find the current through the resistor.
- 2) When the voltage across a resistor is  $120\text{ V}$ , the current through it is  $2.5\text{ mA}$ . Calculate its resistance
- 3) Which of the circuits in the figure below will give you  $V_{ab} = 7\text{ V}$ ?



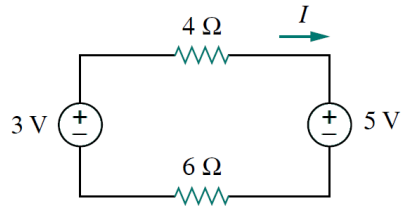
- 4) The current  $I$  in the circuit below is: (a)  $-0.8\text{ A}$  (b)  $-0.2\text{ A}$  (c)  $0.2\text{ A}$  (d)  $0.8\text{ A}$



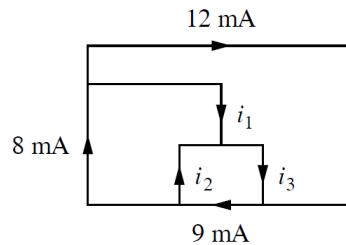
- 5) Use KCL to obtain currents  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit shown below.



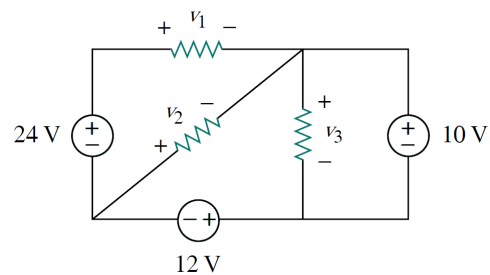
- 6) Obtain  $v_1$  through  $v_3$  in the circuit below.



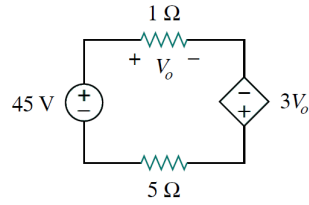
- 7) Calculate the power dissipated in the  $5\text{-}\Omega$  resistor in the circuit below.



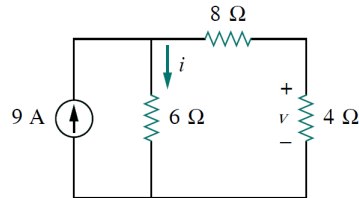
- 8) Find  $i$ ,  $v$ , and the power dissipated in the  $6\text{-}\Omega$  resistor in figure below.



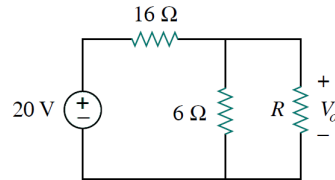
- 9) In the circuit of the figure below, find  $R$  if  $V_o = 4\text{ V}$ .



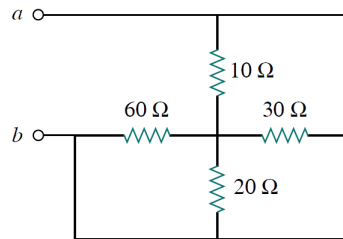
- 10) Obtain the equivalent resistance at the terminals a-b for the circuit shown below.



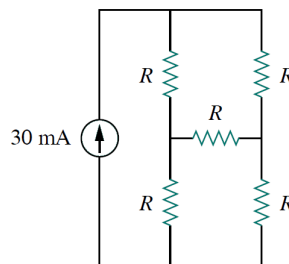- 11) What value of  $R$  in the circuit below would cause the current source to deliver  $800\text{ mW}$  to the resistors?




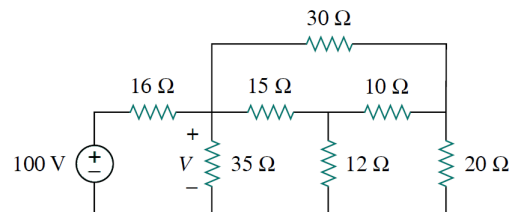- 12) Determine  $V$  in the circuit below.




### Chapter 3

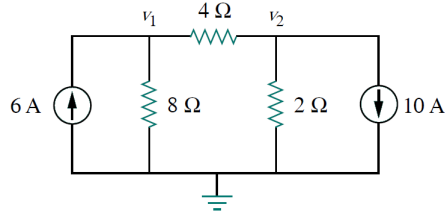
- 13) Determine  $v_1$  and  $v_2$  in the circuit below using nodal analysis.



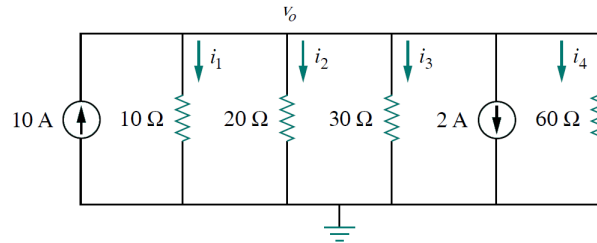
- 14) Find the currents  $i_1$  through  $i_4$  and the voltage  $v_0$  in the circuit shown below using nodal analysis.



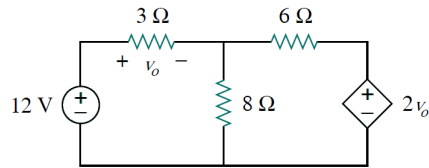
- 15) Calculate  $v_0$  in the circuit shown below using nodal analysis.



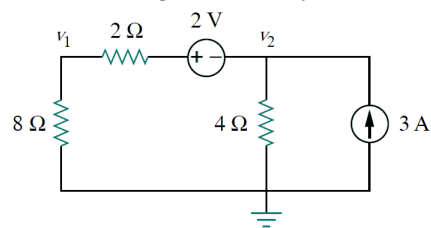
- 16) Calculate  $v_1$  and  $v_2$  in the circuit below using nodal analysis.



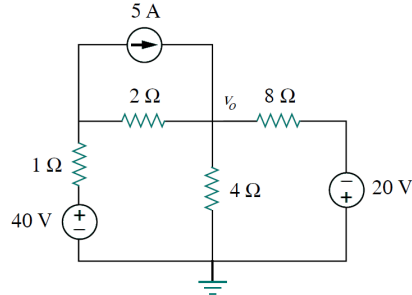
- 17) Apply mesh analysis to find  $v_0$  in the circuit below.



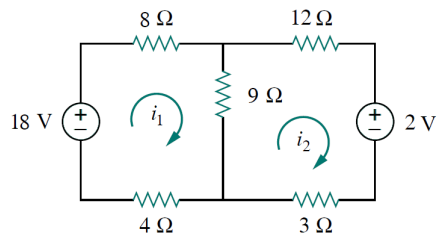
- 18) Calculate the mesh currents  $i_1$  and  $i_2$  in the circuit below.



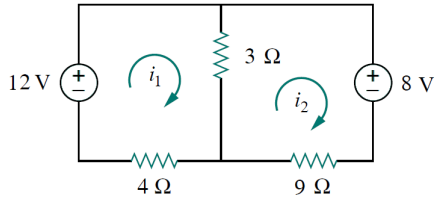- 19) Calculate the mesh currents  $i_1$  and  $i_2$  in the circuit below.




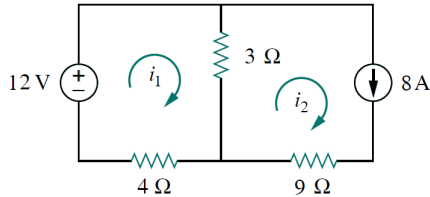- 20) Calculate the mesh currents  $i_1$  and  $i_2$  in the circuit below.




### Chapter 4

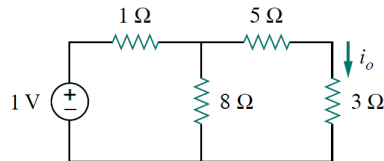
- 21) Calculate the current  $i_o$  in the circuit below. What does this current become when the input voltage is raised to 10 V?



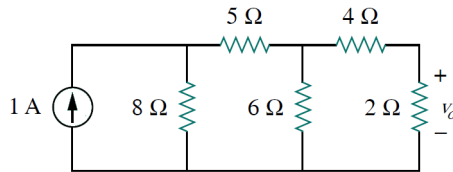
- 22) Find  $v_o$  in the circuit shown below. If the source current is reduced to  $1\ \mu\text{A}$ , what is  $v_o$ ?



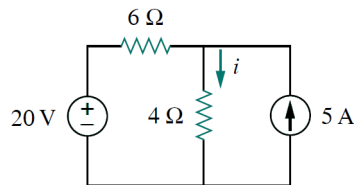
- 23) Apply superposition to find  $i$  in the circuit below.



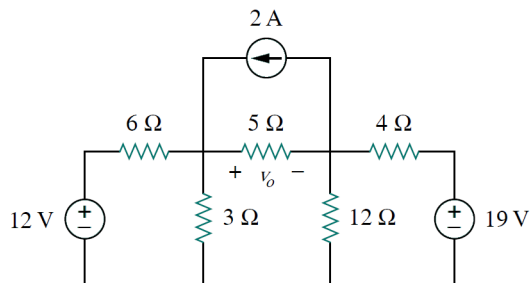
- 24) Determine  $v_o$  in the circuit below using the superposition principle.



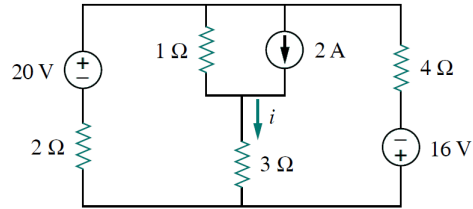
- 25) For the circuit shown below, use superposition to find  $i$ . Calculate the power delivered to the 3-Ω resistor.



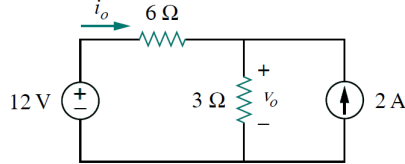
26) Apply source transformation to determine  $v_0$  and  $i_0$  in the circuit below.



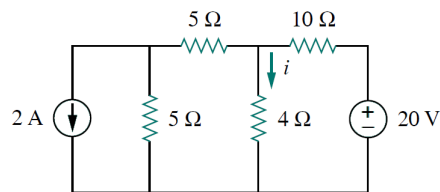
27) For the circuit below, use source transformation to find  $i$ .



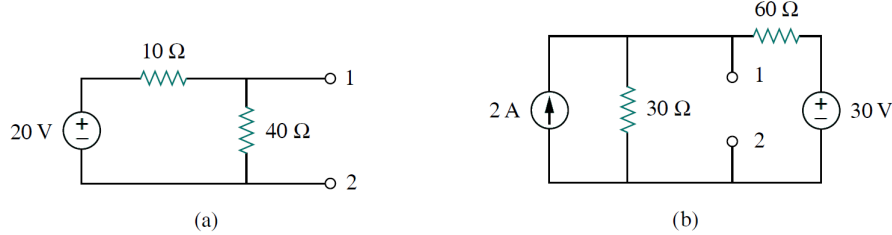28) Determine  $R_{Th}$  and  $V_{Th}$  at terminals 1-2 of each of the circuits below.



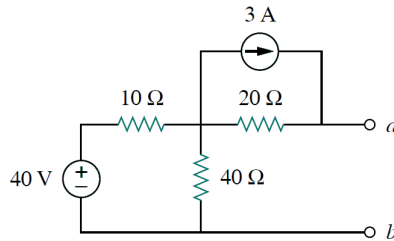29) Find the Thevenin equivalent at terminals a-b of the circuit below.



30) Find the Thevenin equivalent looking into terminals a-b of the circuit below and solve for  $i_x$ .

